
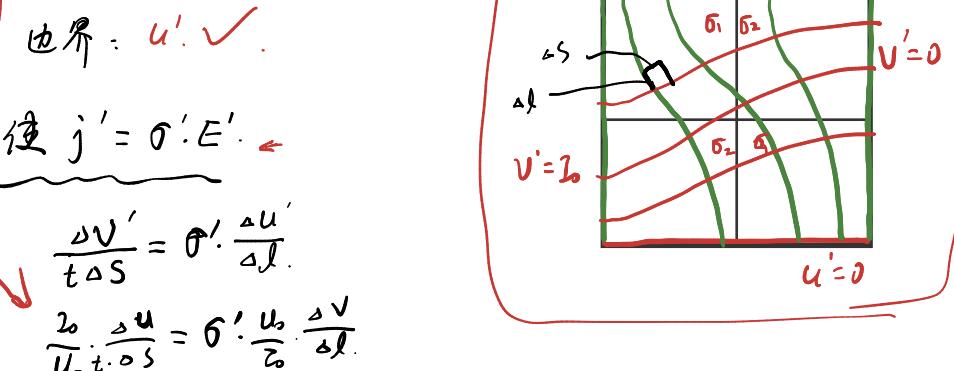


$$\frac{\Delta U}{\Delta S} = E. \quad \frac{\Delta V}{\Delta l \cdot t} = j. \Rightarrow \frac{\Delta V}{\Delta l} = j \cdot t. \quad j \cdot \Delta l = \sigma \cdot E \cdot \Delta l = \Delta I / t.$$

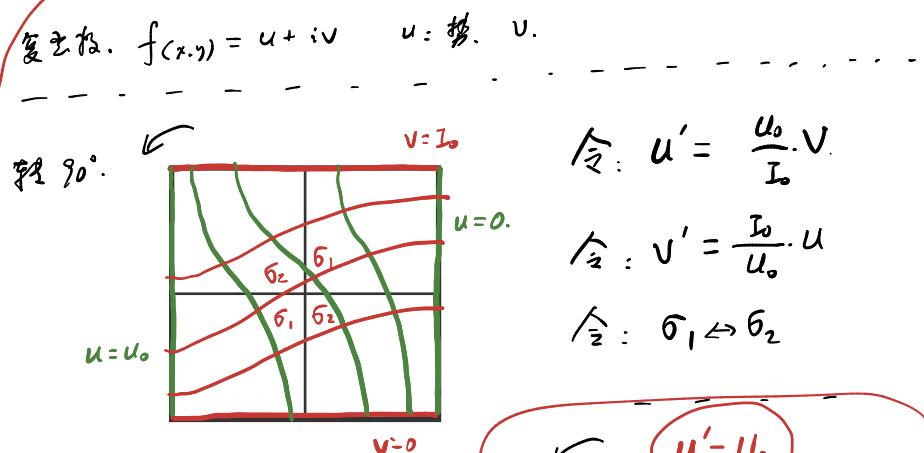$j = \sigma E \Rightarrow \frac{\Delta V}{\Delta l} = t \cdot \sigma \cdot \frac{\Delta U}{\Delta S}$



电容: 基尔霍夫. 节点: $\oint \vec{E} \cdot d\vec{s} = 0 \Rightarrow \sum I = 0$.

回路: $\oint \vec{E} \cdot d\vec{l} = 0 \Rightarrow \sum_{i=1}^F I_i = 0$

网络:

V 个顶点 E 条边. F 个区域.

I: $\left\{ \begin{array}{l} \text{有 } (V-1) \text{ 个独立电压: } U_i, i=1, 2, \dots, (V-1). \\ \Rightarrow \text{有 } (V-1) \text{ 个独立节点方程. } \sum I_{ij} = 0. \end{array} \right.$

II: 设圈电流: $(F-1)$ 个圈电流.


基尔霍夫: $\sum U_{ij} = 0$ $(F-1)$ 个回路方程

III: 设 E 个电流. 循环: $\sum I_{ij} = 0$. $(V-1)$ 个节点.



回路方程: $(F-1)$. $\sum U_{ij} = 0$

$$E = V - 1 + F - 1 = V + F - 2 \quad \leftarrow \text{欧拉公式}$$

简单立方体

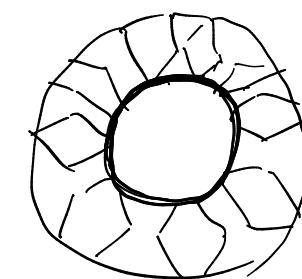


叠加.

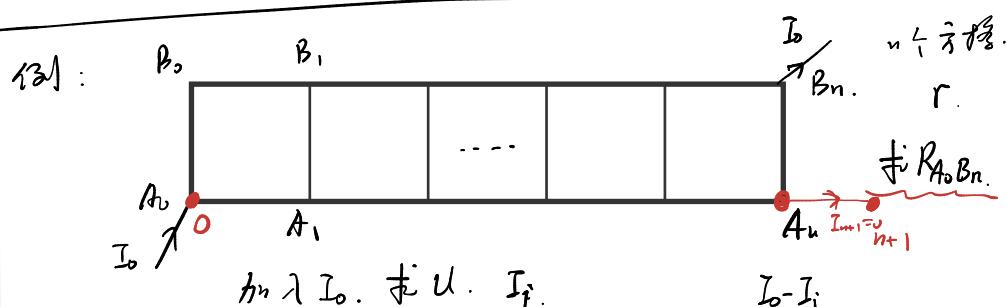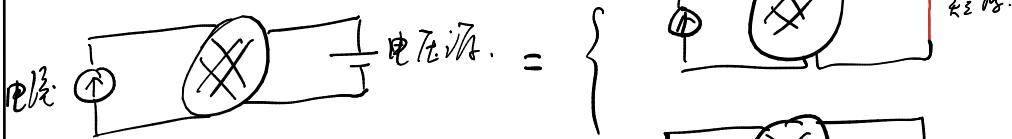

\Rightarrow 回路:

$$I_j + (I_j - I_{j+1}) - (I_0 - I_j) - (I_{j+1} - I_j)^F = 0$$
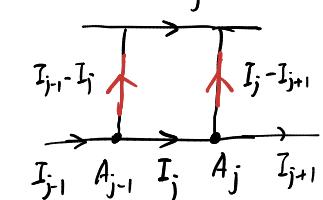
$$\Rightarrow -I_{j-1} + 4I_j - I_{j+1} = I_0. \quad \leftarrow \text{非齐次}$$



$$\text{令 } I_j = \frac{I_0}{2} + a_j, \quad I_{j-1} = \frac{I_0}{2} + a_{j-1}$$

$$\Rightarrow a_{j-1} - 4a_j + a_{j+1} = 0. \quad \leftarrow \text{齐次.} \quad A\lambda^{j-1}$$

$$\text{令 } a_j = A\lambda^j \quad \downarrow \quad 1 - 4\lambda + \lambda^2 = 0.$$

$$\Rightarrow \lambda = \frac{4 \pm \sqrt{12}}{2} = 2 \pm \sqrt{3}.$$



$$\Rightarrow \text{通解: } a_j = A_+ \lambda_+^j + A_- \lambda_-^j$$

$$\text{边界: } I_0 = I_0 \Rightarrow I_0 = \frac{I_0}{2} + a_0 \Rightarrow a_0 = \frac{I_0}{2}$$

$$I_{n+1} = 0 \Rightarrow I_{n+1} = \frac{I_0}{2} + a_{n+1} = 0 \Rightarrow a_{n+1} = -\frac{I_0}{2}.$$

$$\Rightarrow A_+ = \dots = A_- = \dots \Rightarrow I_j = \dots$$
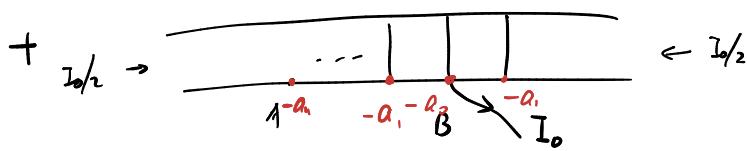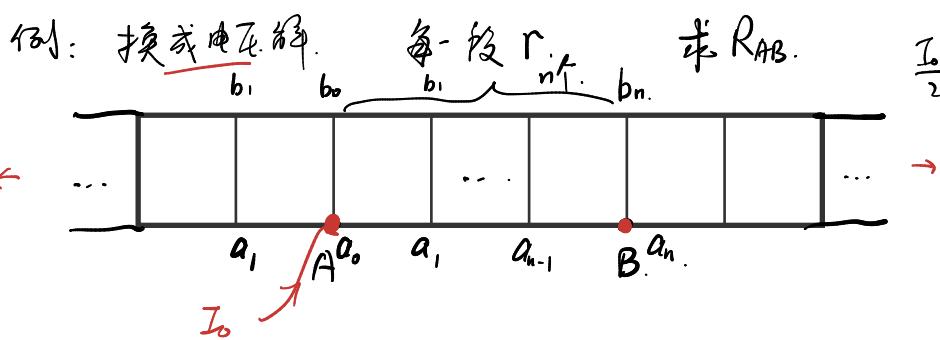
$$U_{A_0 B_n} = \Rightarrow R_{A_0 B_n} = \frac{U_{A_0 B_n}}{I_0}.$$



$$\Rightarrow U_{AB} = 2(a_0 - a_n).$$

考虑:

$$\begin{cases} (a_n - a_{n-1}) + (a_n - a_{n+1}) + (a_n - b_n) = 0. \\ (b_n - b_{n-1}) + (b_n - b_{n+1}) + (b_n - a_n) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} -a_{n-1} + 3a_n - a_{n+1} - b_n = 0 \\ -a_n - b_{n-1} + 3b_n - b_{n+1} = 0 \end{cases}$$

先消去 b . \Rightarrow 差推方程 $b_n = -a_{n-1} + 3a_n + a_{n+1}$

$$\Rightarrow a_{n-2} - 6a_{n-1} + 10a_n - 6a_{n+1} + a_{n+2} = 0. \quad \leftarrow \text{齐次.}$$

$$\text{设 } a_n = A\lambda^n$$

$$\text{代入: } 1 - 6\lambda + 10\lambda^2 - 6\lambda^3 + \lambda^4 = 0.$$

电流全为 0 时. \Rightarrow 电势相等 $\Rightarrow \lambda = 1$.

$$(1-\lambda)(1-5\lambda+5\lambda^2-\lambda^3)=0.$$


$$(1-\lambda)(1-\lambda)(1-4\lambda+\lambda^2)=0.$$

$$\Rightarrow \lambda_1 = 1, \lambda_2 = 1, \lambda_3 = 2 + \sqrt{3}, \lambda_4 = 2 - \sqrt{3}.$$

有重根: $a_n = (\underline{A_1} + nA_2) \cdot \underline{1^n} + A_3 \cdot \lambda_3^n + A_4 \cdot \lambda_4^n$.

边界条件: $n \rightarrow \infty$. 不能取 $A_3 = 0$.
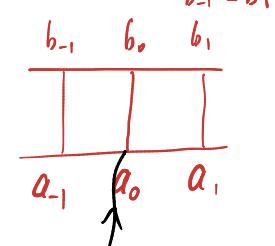
$$n=0, n=1: \quad b_n = -a_{n-1} + 3a_n - a_{n+1}$$



$$\Rightarrow \begin{cases} (a_0 - a_1) + (a_0 - a_1) + (a_0 - b_0) = 1 \\ (b_0 - b_1) + (b_0 - b_1) + (b_0 - a_0) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} a_0 = A_1 + A_4 \\ a_1 = A_1 + A_2 + A_4 \cdot \lambda_4 \end{cases}$$

$$\Rightarrow b_0 = -a_1 + 3a_0 - a_1 = 3A_1 + 3A_4 - 2A_1 - 2A_2 - 2A_4 \lambda_4.$$

$$b_1 = -a_0 + 3a_1 - a_2 = A_1 + A_2 - A_4 + 3A_4 \lambda_4 - A_0 \cdot \lambda_4^2.$$

\Rightarrow 三元一次方程组. \Rightarrow 二元一次 \checkmark .

$$a_n = A_1 + nA_2 + A_4 \cdot \lambda_4^n$$

\checkmark 常数. \leftrightarrow 电势提高. 降低电势. 无用

$$\therefore A_1 = 0.$$

全部为: $\begin{pmatrix} a_n \\ b_n \end{pmatrix} = \begin{pmatrix} A \\ B \end{pmatrix} \cdot \lambda^n$

$$\Rightarrow \begin{cases} (-1+3\lambda-\lambda^2)A - \lambda B = 0 \\ -\lambda A + (-1+3\lambda-\lambda^2)B = 0 \end{cases}$$

要求有非零解: $\frac{-1+3\lambda-\lambda^2}{-\lambda} = \frac{-\lambda}{-1+3\lambda-\lambda^2}$

$$(-1+3\lambda-\lambda^2+\lambda)(-1+3\lambda-\lambda^2-\lambda) = 0.$$

$$\Rightarrow \underbrace{\lambda_{1,2}}_{\text{齐次}} = 1, \quad \lambda_{3,4} = 2 \pm \sqrt{3}.$$

$$\text{对 } \lambda_{1,2}: \quad -1+3\lambda-\lambda^2 = 1 \Rightarrow \begin{cases} A - B = 0 \\ -A + B = 0 \end{cases} \Rightarrow A = B.$$


$$\text{对 } \lambda_{3,4}: \quad -1+3\lambda-\lambda^2 = -1 \Rightarrow \begin{cases} -\lambda A - \lambda B = 0 \\ -\lambda A - \lambda B = 0 \end{cases} \Rightarrow A = -B.$$

$$\Rightarrow \begin{pmatrix} a_n \\ b_n \end{pmatrix} = [A_1 \begin{pmatrix} 1 \\ 1 \end{pmatrix} + nA_2 \begin{pmatrix} 1 \\ 1 \end{pmatrix}] \cdot 1^n + A_3 \begin{pmatrix} 1 \\ -1 \end{pmatrix} \lambda_3^n + A_4 \begin{pmatrix} 1 \\ -1 \end{pmatrix} \lambda_4^n$$

再用边界条件.


例题. 二端响应函数

r , 求 $U_{AB} = ?$

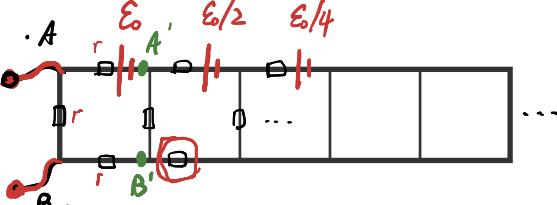

电压源原理: 原电源: $A \xrightarrow{U_{AB}} B$

$$r_o = R_{AB}$$

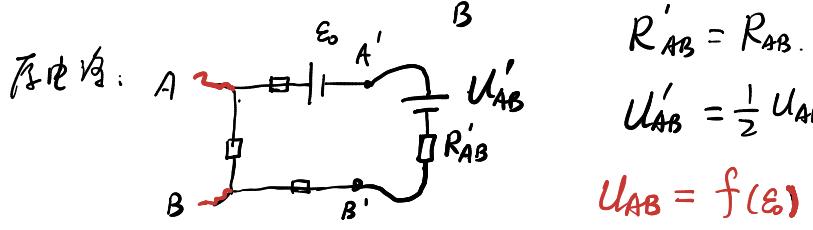

$$R_{AB} = (R_{AB} + 2r) // r \Rightarrow R_{AB} = (\sqrt{3}-1)r = \text{约 } 0.73E$$

$$U_{AB} = r \cdot \frac{E_0 + \frac{1}{2}U_{AB}}{3r + R_{AB}} \Rightarrow U_{AB} = \frac{\frac{r}{3r+R_{AB}} \cdot E_0}{1 - \frac{1}{2} \cdot \frac{r}{3r+R_{AB}}}$$

力学中 \perp = 二端响应函数.

光滑球, r, m, θ .

静止. 释放. 求 N

$$a=0$$

① 地面上看. "O" $\Rightarrow N$.

② 在地球上看. 牛顿第二定律:

$$g' = g - a'$$

$$N = f(g) = 0 \cdot mg$$

$$N' = f(g') = 0 \cdot mg'$$

$$N' = \frac{g-a'}{g} \cdot N \oplus$$

$$\text{解: } a_y = \frac{a'}{2}$$

$$\text{解: } a_{A0} \text{ 沿球切向} \Rightarrow a_x \cdot \sin\theta = a_y \cdot \cos\theta$$

$$\Rightarrow a_x = \frac{\cos\theta}{\sin\theta} \cdot \frac{a'}{2}$$

$$\text{对 "O" 点: } 2F \cdot \cos\theta = N \Rightarrow F = \frac{N-mg}{2\cos\theta}$$


$$\text{解: } N' = 2F \cdot \cos\theta \Rightarrow F = \frac{N'}{2\cos\theta}$$

$$\Rightarrow \text{对 } A \text{ 点: } F' \cdot \cos\theta + mg - F \cdot \cos\theta = m \cdot a_y \quad \text{①}$$

$$\text{解: } F' \cdot \sin\theta + F \cdot \sin\theta = m \cdot a_x \Rightarrow a_x \quad \text{②}$$

解得 \perp - ✓

三端网络 (线性)

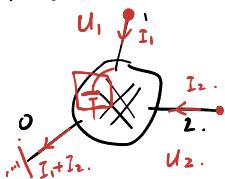


$$U_1 = f_1(I_1, I_2) = U_0 + a_{11}I_1 + a_{12}I_2$$

$$U_2 = f_2(I_1, I_2) = U_0 + a_{21}I_1 + a_{22}I_2$$




$$a_{12} = a_{21} \Rightarrow \text{三端网 } \perp$$

无 \perp : 三个自由度 \Rightarrow 入或 \triangle

有 \perp : 三个 + 两个 \Rightarrow

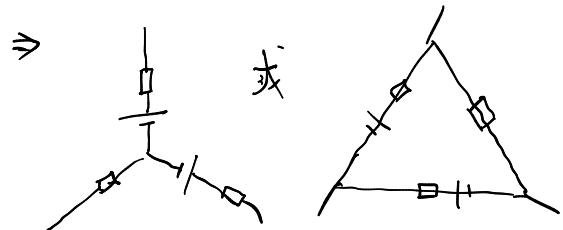


结:

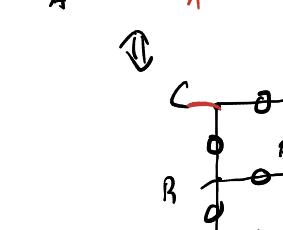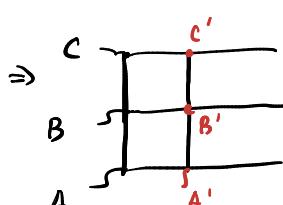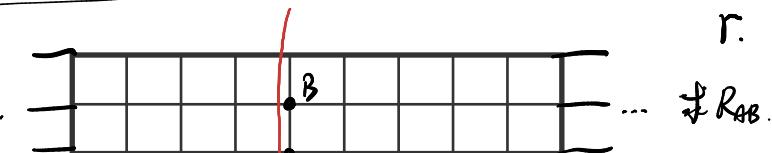

$$R_{AC} = 2y = (2y+2) // 2$$

$$R_{AB} = x+y = \dots$$

例:

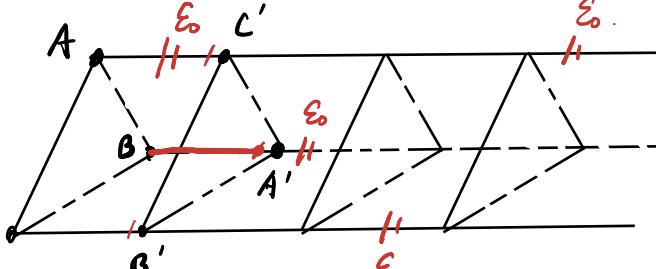

求 U_{AC}


电压网 \perp :

$$U_{AC} =$$

$$\Rightarrow R_{AB} = 2x = \frac{2}{3} // (2x+2)$$


$$\Rightarrow x = \frac{-3+\sqrt{21}}{2}$$

再入电源:

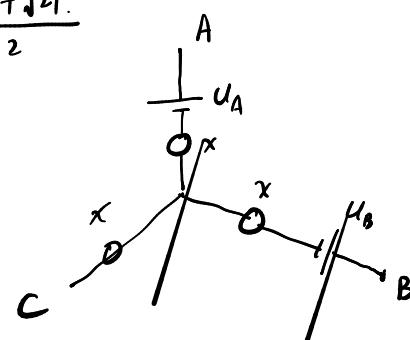

又. 互网电压关系:

$$U_{A'} = U_A \quad U_{B'} = U_B$$

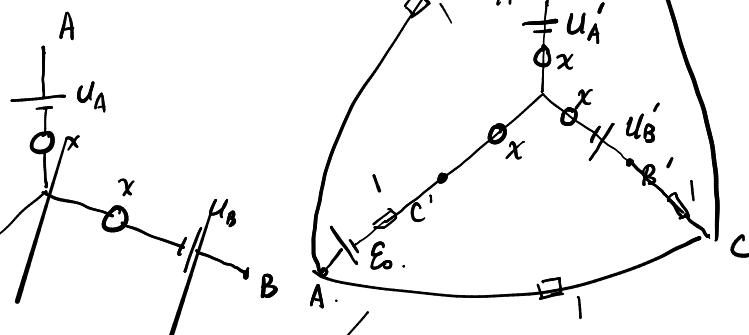

$$\Rightarrow U_{AC} = U_A. \quad \text{叠加原理:}$$

$$U_{BC} = U_B.$$

①. 有 E_0 : $\begin{cases} U_{AC1} = 1 \cdot E_0 \cdot \left(\frac{x+2}{2} + x+1\right)^{-1} \cdot \frac{1}{2} \\ U_{BC1} = 0. \end{cases}$

②. 有 U_A : $\begin{cases} U_{AC2} = 0 \\ U_{BC2} = 1 \cdot U_A \cdot \left(\frac{x+2}{2} + x+1\right)^{-1} \cdot \frac{1}{2} \end{cases}$

③. 有 U_B : $\begin{cases} U_{AC3} = -1 \cdot U_B \cdot \left(\frac{x+2}{2} + x+1\right)^{-1} \cdot \frac{1}{2} \\ U_{BC3} = -1 \cdot U_B \cdot \left(\frac{x+2}{2} + x+1\right)^{-1} \cdot \frac{1}{2}. \end{cases}$

$$\Rightarrow U_{AC} = U_A = \lambda E_0 + 0 - \lambda U_B. \quad ①$$

$$U_{BC} = U_B = 0 + \lambda U_A - \lambda U_B. \quad ②$$


$$\Rightarrow (1+\lambda) U_B = \lambda (\lambda E_0 - \lambda U_B).$$

$$\Rightarrow U_B = \frac{\lambda^2 E_0}{1+\lambda+\lambda^2}.$$

$$\Rightarrow U_A = \frac{(\lambda+\lambda^2+\lambda^3) E_0 - \lambda^3 E_0}{1+\lambda+\lambda^2} = \frac{(\lambda+1) E_0}{1+\lambda+\lambda^2}.$$

$$\Rightarrow U_{AC} = U_A = \dots$$

4端网络:

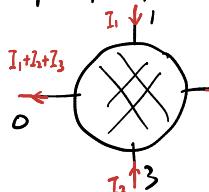


电阻网络: 自由度为6

试: $\begin{array}{c} \text{图1} \\ \neq \end{array} \quad \begin{array}{c} \text{图2} \\ \Leftrightarrow \end{array} \quad \begin{array}{c} \text{图3} \\ \Leftrightarrow \end{array}$

$$\begin{cases} U_1 = U_{10} + a_{11}I_1 + a_{12}I_2 + a_{13}I_3. \\ U_2 = U_{20} + a_{21}I_1 + a_{22}I_2 + a_{23}I_3. \\ U_3 = U_{30} + a_{31}I_1 + a_{32}I_2 + a_{33}I_3. \end{cases}$$



例:

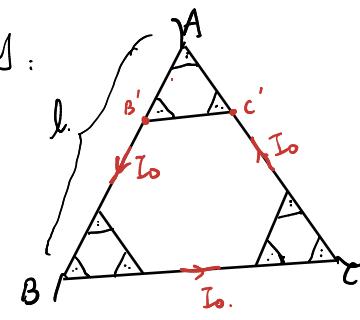

(1). 已知. 单位长电阻 λ . 求 R_{AC} .

(2). $B = kt$. 求 I_0 .

(1) 原图:

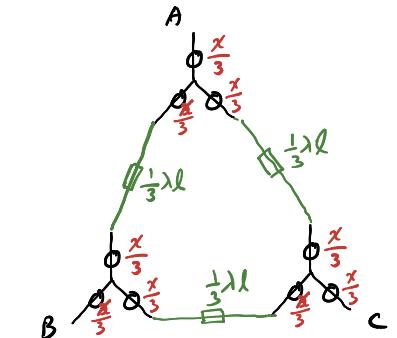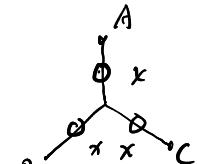


$$\Rightarrow R_{AC} = 2x = \frac{2}{3}x + \left(\frac{2}{3}x + \frac{1}{3}\right) / \left(\frac{4}{3}x + \frac{2}{3}\right).$$

$$\Rightarrow x = \frac{1}{4}\lambda l. \quad \Rightarrow R_{AC} = 2x = \frac{1}{2}\lambda l.$$

无量纲化: $x = \frac{1}{4}$.

(2). 从最外层等效到内层 \sim 关系时. 只能看电流、电压, 不包含电动势.

只看电阻产生的电压降. 输入输出是 I .

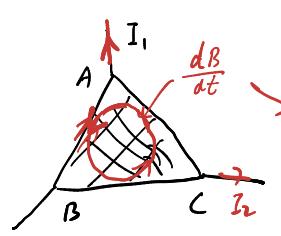

$$E_{BA}: \text{从 } B \rightarrow A. \quad \sum I r.$$

$$E_{BC}: \text{从 } B \rightarrow C. \quad \sum I r.$$

$$E_{BA} = a_{11}I_1 + a_{12}I_2 + E_{10} \quad \downarrow \frac{dB}{dt}$$

$$E_{BC} = a_{21}I_1 + a_{22}I_2 + E_{20}.$$

$a_{ij} \rightarrow E_{10}, E_{20}$. 相互独立. (叠加原理)

先 a_{ij} : 无 $\frac{dB}{dt}$ \Rightarrow

$$a_{11} = \frac{1}{2} = a_{22}. \quad a_{12} = a_{21} = \frac{1}{4}.$$

由 $\frac{dB}{dt}$ 产生的部分:

$$E_0 = k \cdot S_E = k \cdot \frac{\sqrt{3}}{4} l^2.$$

$$E_{BA} = E_0 = -\frac{1}{3}E_0.$$

$$E_{BC} = E_{20} = \frac{1}{3}E_0.$$

\Rightarrow 对于最外层:

$$\begin{cases} E_{BA} = \frac{1}{2}I_1 + \frac{1}{4}I_2 - \frac{1}{3}E_0 \\ E_{BC} = \frac{1}{4}I_1 + \frac{1}{2}I_2 + \frac{1}{3}E_0. \end{cases}$$


对次外层: $x \rightarrow \frac{1}{3}x, S \rightarrow \frac{1}{9}S, E_0 \rightarrow \frac{1}{3}E_0$

$$E'_{BA} = \frac{1}{6}I_1 + \frac{1}{12}I_2 - \frac{1}{27}E_0$$

$$E'_{BC} = \frac{1}{12}I_1 + \frac{1}{6}I_2 + \frac{1}{27}E_0.$$

求最外层总电压降.

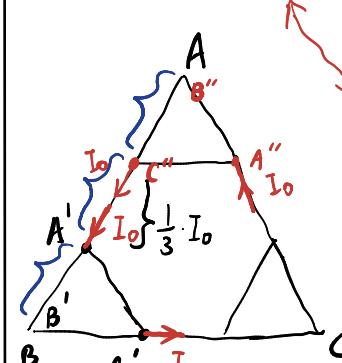
$$\begin{cases} E'_{BC''} = \frac{1}{12}(-I_0) + \frac{1}{6}I_0 + \frac{1}{27}E_0 \\ E'_{CA'} = \frac{1}{3}I_0. \\ E'_{AB'} = -E'_{BA'} = -\left[\frac{1}{6}(-I_0) + \frac{1}{12}I_0 - \frac{1}{27}E_0\right] \end{cases}$$



$$\Rightarrow E_{A \rightarrow B \rightarrow C \rightarrow A} = 3 \cdot (E_{B''C''} + E_{C''A'} + E_{A'B'}) \stackrel{\text{基二}}{=} E_0.$$

$$\Rightarrow I_0 = \frac{14}{27} E_0. \Rightarrow I_0 = \frac{14}{27} \cdot \frac{E_0}{\lambda l}$$

例：N维立方体，r, 求 R_M .

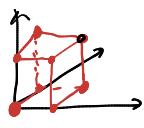

顶点: $(0, 0, \dots, 0)$ $\underbrace{(1, 1, \dots, 1)}_{N}$
相邻: $\uparrow N$

C_N^1 : $(1, 0, \dots, 0)$ 或 $(0, 1, 0, \dots, 0)$ 或 \dots $(0, 0, \dots, 0, 1)$.


定义. 顶点之间间隔: M: $A \rightarrow B$. 最少步数. $1 \leq M \leq N$.

A : $(0, 0, \dots, 0)$, B 点: $(0, 0, \dots, 0, \underbrace{1, 1, \dots, 1})_{M+1}$

利用叠加原理:

(1) 从 A 输入 I_0 , 从其余边平均输出一份电流: $\frac{I_0}{2^{N-1}} = \Delta I$.

对 N 维立方体: 线数: N , 顶点数: 2^N . U_{AB1}

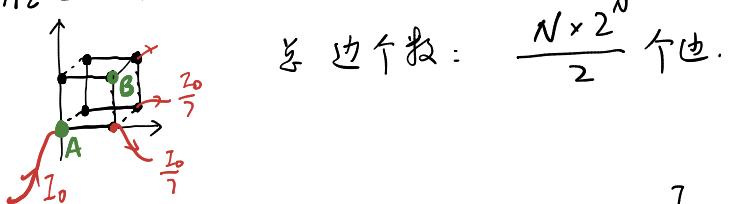

(2) 从 B 输出 I_0 , 从其余边平均输出一份电流: $\frac{I_0}{2^{N-1}} = \Delta I$.

$\Downarrow U_{AB2}$.

$$U_{AE1} = U_{AB2}. \Rightarrow U_{AB} = 2U_{AB1} \Rightarrow R_M = R_{AB} = \frac{2U_{AB1}}{I_0 + \Delta I}.$$

\boxed{A} $(0, 0, \dots, 0)$. 出发 $\begin{cases} (1, 0, 0, \dots, 0) \\ (0, 1, 0, \dots, 0) \\ (0, 0, 1, \dots, 0) \end{cases}$
间隔: 为 1 个点.

"1": 点个数: C_N^1 个; 边个数: $C_N^1 \uparrow$
 \downarrow 间隔 $\approx 2^{N-1}$

"2": 点个数: C_N^2 个; 边个数: $(N-1) \cdot C_N^1$
 \downarrow $C_N^2 \Delta I$

"3": 点个数: C_N^3 个; 边个数: $(N-2) \cdot C_N^2$.

"M": 点个数: C_N^M 个; 边个数: $(N-M+1) \cdot C_N^{M-1}$

"M+1": \dots

$$\Rightarrow U_{AB1} = \sum_{i=0}^{M-1} \frac{r}{C_N^i \cdot (N-i)} \cdot (I_0 - \sum_{j=1}^i C_N^j \cdot \frac{I_0}{2^{N-1}}).$$

$$\Rightarrow R_{AB} = \frac{2U_{AB1}}{I_0 + \frac{1}{2^{N-1}} I_0}$$

例: 正十二面体. 邻边: r, 求 顶2点之间电阻.

求 R_{AB} , R_{AE} .



(1) 从 A 注入 I_0 .
从余下边流出.

$$\lambda \cdot \frac{1}{19} I_0 \Rightarrow U_{AE1}$$

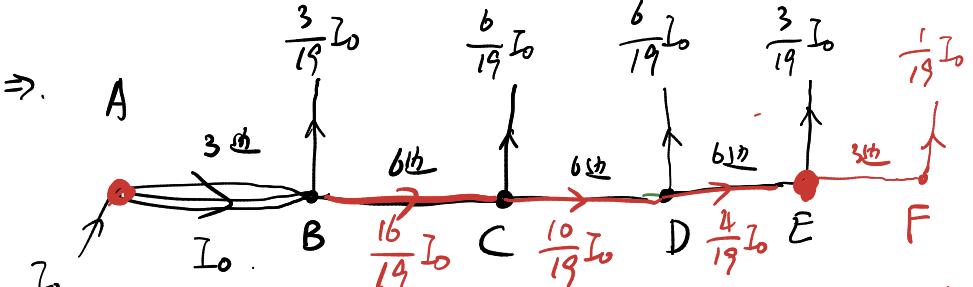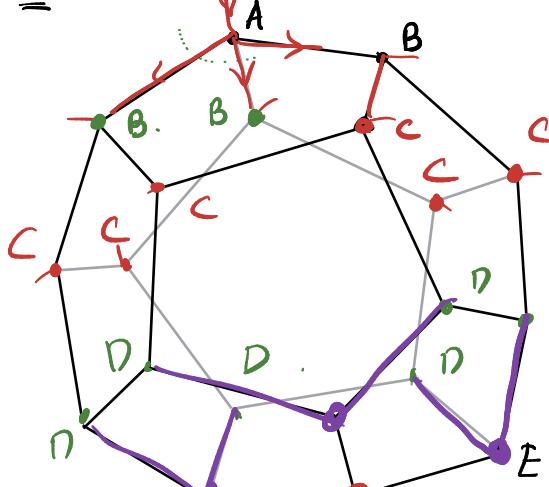(2) 从 E 注入 I_0 .
从余下边流出.

$$\lambda \cdot \frac{1}{19} I_0 \Rightarrow U_{AE2}$$

$$\Rightarrow U_{AE} = U_{AE1} = U_{AE2} = 2U_{AE1}.$$



$$\Rightarrow U_{AE1} = I_0 \cdot \frac{r}{3} + \frac{16}{19} I_0 \times \frac{1}{6} r + \frac{10}{19} I_0 \times \frac{r}{6} + \frac{4}{19} I_0 \times \frac{r}{6}.$$

$$\Rightarrow \dots \Rightarrow R_{AE} = \frac{17}{15} r.$$


静磁场:

B-S. $I \rightarrow B$.

$$\vec{dB} = \frac{\mu_0}{4\pi} \cdot \frac{I \cdot d\vec{l} \times \hat{r}}{r^2}$$

$$\Rightarrow \int \vec{B} \cdot d\vec{s} = 0. \quad \int \vec{B} \cdot d\vec{l} = \mu_0 \cdot \sum I_{\text{内}}$$
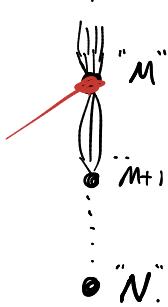
$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \cdot I_1 - I_2.$$



18]. $\rho \ll r$. $B(p)$

保留一阶 \Rightarrow 没了.

\Rightarrow 得到 $= P_1$

$$\Rightarrow B = \frac{\mu_0 I}{4\pi} \int \frac{rd\theta \cdot \hat{r} \times \hat{r}_1}{r^2 + \rho^2 - 2r\rho \cos\theta}$$

$$|\hat{r} \times \hat{r}_1| = \cos\delta = 1 - \frac{\rho^2}{r^2} = 1 - \frac{1}{2} \left(\frac{\rho \sin\theta}{r} + O(2) \right)^2$$

$$= 1 - \frac{1}{2} \left(\frac{\rho^2 \sin^2\theta}{r^2} + O(4) + O(3) \right)$$

$$= 1 - \frac{1}{2} \frac{\rho^2 \sin^2\theta}{r^2}$$

$$\text{或: } \cos\delta = \frac{-\rho^2 + r^2 + (r^2 + \rho^2 - 2r\rho \cos\theta)}{r \cdot \sqrt{r^2 + \rho^2 - 2r\rho \cos\theta}}$$

$\approx \dots$

$$\Rightarrow B = \frac{\mu_0 I}{4\pi} \int_0^{2\pi} r d\theta \left(1 - \frac{1}{2} \frac{\rho^2 \sin^2\theta}{r^2} \right) \cdot \frac{1}{r^2} \left(1 + \frac{\rho^2}{r^2} - \frac{2\rho}{r} \cos\theta \right)^{-1}$$


$$= \frac{\mu_0 I}{4\pi r} \int_0^{2\pi} d\theta \left(1 - \frac{1}{2} \frac{\rho^2 \sin^2\theta}{r^2} \right) \left[1 + (-1) \left(\frac{\rho^2}{r^2} - \frac{2\rho}{r} \cos\theta \right) + \frac{(-1)(-1)}{2} \left(\frac{2\rho}{r} \cos\theta \right)^2 \right]$$

$$= \frac{\mu_0 I}{4\pi r} \int_0^{2\pi} d\theta \left(1 - \frac{1}{2} \frac{\rho^2 \sin^2\theta}{r^2} \right) \left[1 + \frac{2\rho}{r} \cos\theta - \frac{\rho^2}{r^2} + \frac{4\rho^2}{r^2} \cos^2\theta \right]$$


$$= \frac{\mu_0 I}{4\pi r} \int_0^{2\pi} d\theta \left[1 + \frac{2\rho}{r} \cos\theta - \frac{\rho^2}{r^2} + \frac{4\rho^2}{r^2} \cos^2\theta - \frac{1}{2} \frac{\rho^2 \sin^2\theta}{r^2} \right]_{0}^{\frac{1}{2}\pi} \Big|_{\frac{1}{2}\pi}^{2\pi}$$

$$= \frac{\mu_0 I}{4\pi r} \cdot (2\pi - \frac{\rho^2}{r^2} \cdot 2\pi + \frac{4\rho^2}{r^2} \cdot \pi - \frac{1}{2} \frac{\rho^2}{r^2} \cdot \pi)$$

$$= \dots \checkmark$$

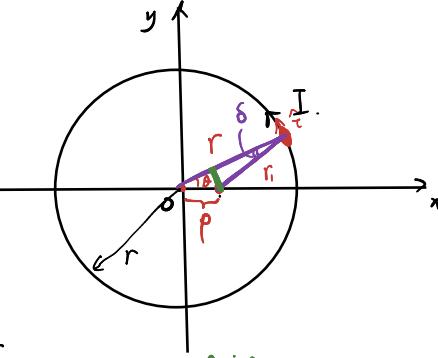

Yth. \Rightarrow i.e. A.

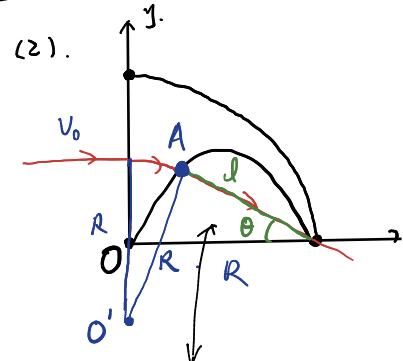

$$A: \begin{cases} x = R \sin\theta \\ y = l(\theta) \sin\theta \end{cases}$$


$$x = R - l \cos\theta = R \sin\theta$$

$$\Rightarrow l = \frac{1 - \sin\theta}{\cos\theta} \cdot R$$

$$S_B = \int y_A \cdot dx_A = \int l \sin\theta \cdot R d(\sin\theta)$$

$$= \int_0^{\frac{\pi}{2}} \frac{(1 - \sin\theta) \sin\theta}{\cos\theta} \cdot R^2 \cos\theta d\theta$$
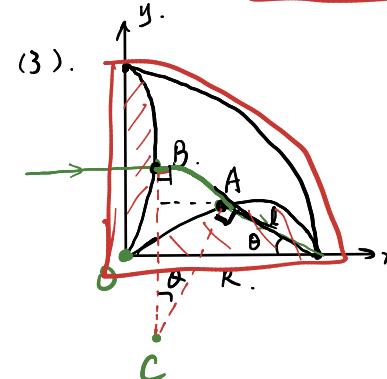
$$= R^2 \left(1 - \frac{\pi}{4} \right) \Rightarrow S = \frac{\pi}{4} R^2 S_B = \left(\frac{\pi}{2} - 1 \right) R^2$$



$$A: \begin{cases} x_A = R - l \cos\theta \\ y_A = l \sin\theta \end{cases} \quad l = l(\theta)$$

$$C: \begin{cases} x_C = R - l \cos\theta - R \sin\theta \\ y_C = l \sin\theta - R \cos\theta \end{cases}$$

$$B: \begin{cases} x_B = R - l \cos\theta - R \sin\theta \\ y_B = l \sin\theta - R \cos\theta + R \end{cases}$$

$$\Rightarrow S_B = \int x_B \cdot dy_B + \int y_A \cdot dx_A$$

$$= \int (R - l \cos\theta - R \sin\theta) \cdot d(l \sin\theta - R \cos\theta)$$

$$+ \int l \sin\theta \cdot d(-l \cos\theta)$$

$$= - \int l \sin\theta \cdot d(l \cos\theta) + \int [R d(l \sin\theta) - R^2 d \cos\theta - l \cos\theta d(l \sin\theta)]$$

$$+ l \cdot \cos\theta \cdot R d \cos\theta - R \sin\theta d(l \sin\theta) + R^2 \sin\theta d \cos\theta$$

$$l^{(1)}: \int_0^{\frac{\pi}{2}} R^2 d \cos\theta + R^2 \sin\theta d \cos\theta = R^2 - \int_0^{\frac{\pi}{2}} R^2 \sin\theta \sin\theta d\theta$$

$$= R^2 - \frac{\pi}{4} R^2 = (1 - \frac{\pi}{4}) R^2$$

$$l^{(1)}: \int_0^{\frac{\pi}{2}} R d(l \sin\theta) + l \cos\theta \cdot R d \cos\theta - R \sin\theta d(l \sin\theta)$$

$$= \int_0^{\frac{\pi}{2}} R (1 - \sin\theta) d(l \sin\theta) + l \cos\theta \cdot R d \cos\theta$$

$$\stackrel{\text{分部}}{=} R (1 - \sin\theta) \cdot l \sin\theta \Big|_0^{\frac{\pi}{2}} + \int_0^{\frac{\pi}{2}} l \sin\theta d(+R \sin\theta) + \int_0^{\frac{\pi}{2}} l \cos\theta R d \cos\theta$$


$$= \int_0^{\frac{\pi}{2}} l \cdot \sin\theta \cos\theta \cdot R d\theta - \int_0^{\frac{\pi}{2}} l \cdot \cos\theta \cdot R \cdot \sin\theta d\theta = 0$$

$$l^{(2)}: - \int l \sin\theta d(l \cos\theta) - \int l \cos\theta d(l \sin\theta)$$

$$\stackrel{\text{分部}}{=} - l \sin\theta \cos\theta \Big|_0^{\frac{\pi}{2}} + \int l \cos\theta d(l \sin\theta) - \int l \cos\theta d(l \sin\theta)$$

$$= 0$$

19]. 求磁感线形状.

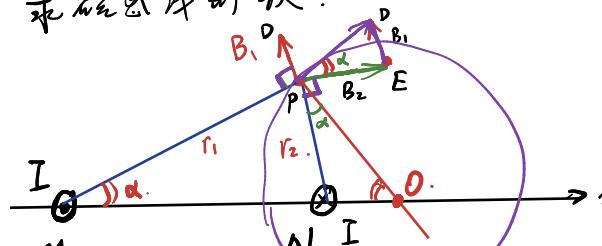

$$PE = \frac{\mu_0 I}{2\pi r_1}, ED' = \frac{\mu_0 I}{2\pi r_2} \Rightarrow \frac{PE}{ED'} = \frac{r_1}{r_2} \quad \text{且} \angle E = \angle MPN$$

$\Rightarrow \Delta PED' \sim \Delta MPN$.

$\angle O = \angle O, \angle OPN = \angle OMP \Rightarrow \Delta MOP \sim \Delta PON$.

$$\frac{MO}{PO} = \frac{PO}{NO} \Rightarrow MO \cdot NO = PO^2 \Rightarrow \text{Apollonius 定理}$$


粒子在磁场中运动.

$$v_0 \Rightarrow R = \frac{mv_0}{qB}$$

求最小磁感应强度.

$$S = 2 \cdot \left(\frac{\pi}{4} R^2 - \frac{1}{2} R^2 \right) = \left(\frac{\pi}{2} - 1 \right) R^2$$

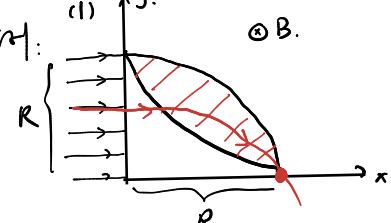参考题: 证明: 对于一个带电粒子在匀强磁场中的运动, 其面积为 $S = (\frac{\pi}{2} - 1) R^2$.



(4) y_{th} . 大冲. 莫培督原理. 即道.

$M \rightarrow N$. 速度分布与力学原理.

分析作用:

$$S_0 = \int \sum p_i dq_i = \text{常数}$$

$$L = \frac{1}{2} m(x^2 + y^2) + q \vec{v} \cdot \vec{A}$$

$$\vec{p} = m\vec{v} + q\vec{A}$$

$$\Rightarrow S_0 = \int (m\vec{v} + q\vec{A}) \cdot d\vec{l}$$

$$= \int m\vec{v} \cdot \vec{v} dt + \int q\vec{A} \cdot d\vec{l}$$

$$= m v_0^2 t + \int q\vec{A} \cdot d\vec{l}$$

$$S_{MPN} = m v_0^2 \frac{2R}{v_0} + \int_{MPN} q\vec{A} \cdot d\vec{l}$$

$$S_{MQN} = m v_0^2 \frac{\pi R}{v_0} + \int_{MQN} q\vec{A} \cdot d\vec{l}$$

$$\Rightarrow - \int_{MQN} q\vec{A} \cdot d\vec{l} + \int_{MPN} q\vec{A} \cdot d\vec{l} = \oint q\vec{A} \cdot d\vec{l} = m v_0^2 \frac{R}{v_0} (\pi - 2)$$

$$\frac{m v_0}{qB} = R \quad = qBR^2(\pi - 2)$$


$$\text{又: } \oint \vec{A} \cdot d\vec{l} = \iint \vec{B} \cdot d\vec{s} = B \cdot 2S$$

$$\Rightarrow S = R^2 (\frac{\pi}{2} - 1)$$

例: 正交电场. 磁场. 考虑相对论.

$$\vec{B} = -B\hat{z}, \vec{E} = -E\hat{y}$$

原点静止释放. 求轨迹.

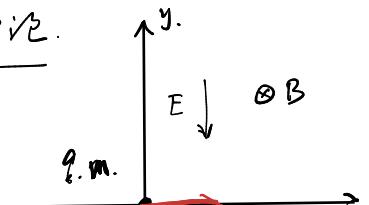

$$(1) \text{ 经典情形. } \frac{dp_x}{dt} = -qBv_y \Rightarrow \frac{d}{dt}(p_x + qBy) = 0$$

$$P_x = p_x + qBy \Rightarrow P_x \text{ 为常数. 表现为匀速直线运动.}$$

$$\begin{cases} p_x + qBy = 0 \\ E = 0 + -qE \cdot y = \frac{p_x^2 + p_y^2}{2m} \Rightarrow p_y \end{cases} \Rightarrow \text{积分} \Rightarrow \text{抛物线}$$

$$(2) \text{ 相对论情形. } \Rightarrow \underline{p_x + qBy = 0}$$

$$\text{能量: } E = \sqrt{m_0 c^2 + p_x^2 + p_y^2} = \sqrt{(m_0 c^2)^2 + (p_x^2 + p_y^2) c^2}$$

$$p_x, p_y \Rightarrow \text{轨迹. } \Rightarrow$$